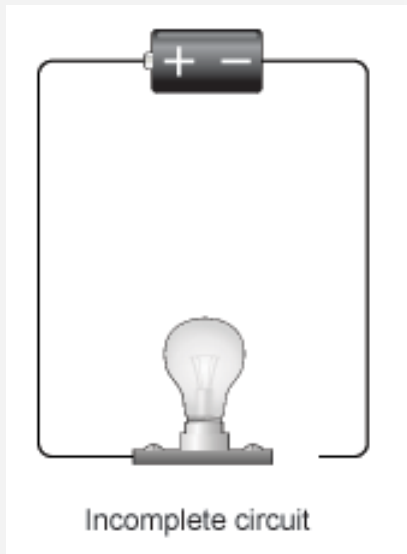


# **18.4**

## **Electrical Circuits**

# Electrical Circuits

- An electric circuit is a **complete path** through which a charge can flow.
- For the charge to flow, the path must be a **complete loop**.





# Circuit Diagram




- Circuit diagrams use **symbols** to represent parts of a circuit, including a **source** of electrical energy and **devices** that are run by the electrical energy.
- In a simple circuit a **battery** provides the energy to operate a device such as a **bell** or a **light bulb**.
- A circuit diagram shows the possible **complete paths** in which charge can flow.
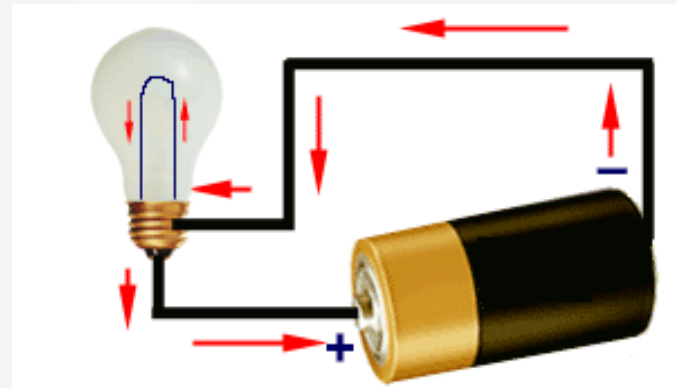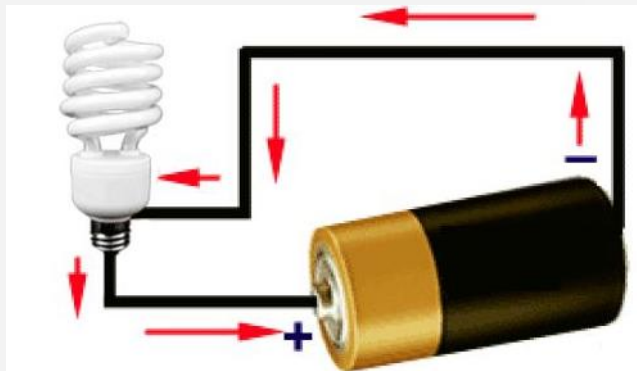
# Circuit Diagram

In the figure below, show an electrical circuit. The “+” and the “-“ on the battery indicate the positive and negative terminals. Arrows show the direction of current, from negative to positive. (Remember; the charge flowing thru the circuit is the electrons which has a “-“ charge.)



# Circuit Diagram

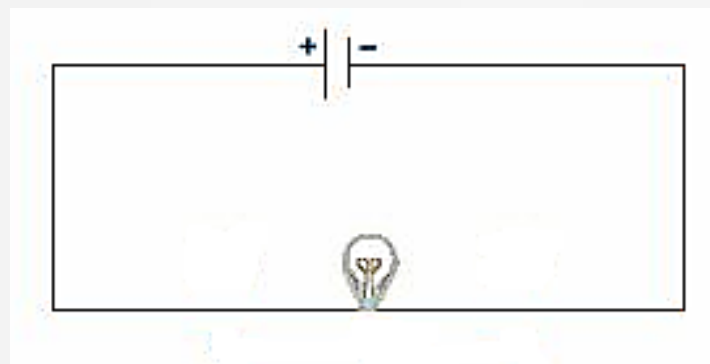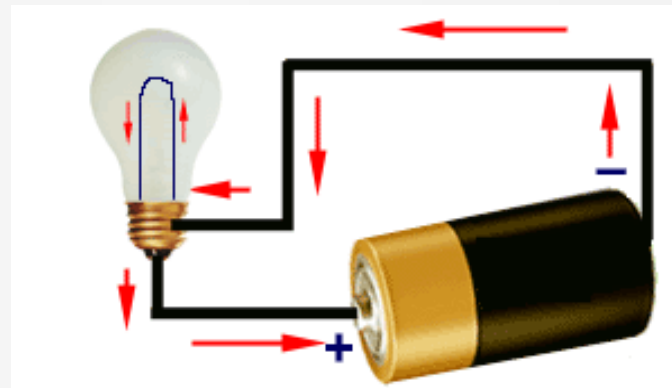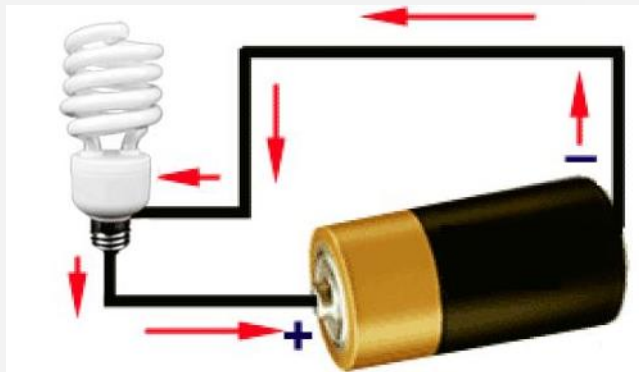


# Series Circuits

- In a series circuit, charge has only **one path** through which it can flow.
- If **one** element stops functioning in a series circuit, **none** of the elements can operate.


# Series Circuits

Example:

Old Christmas Tree Lights

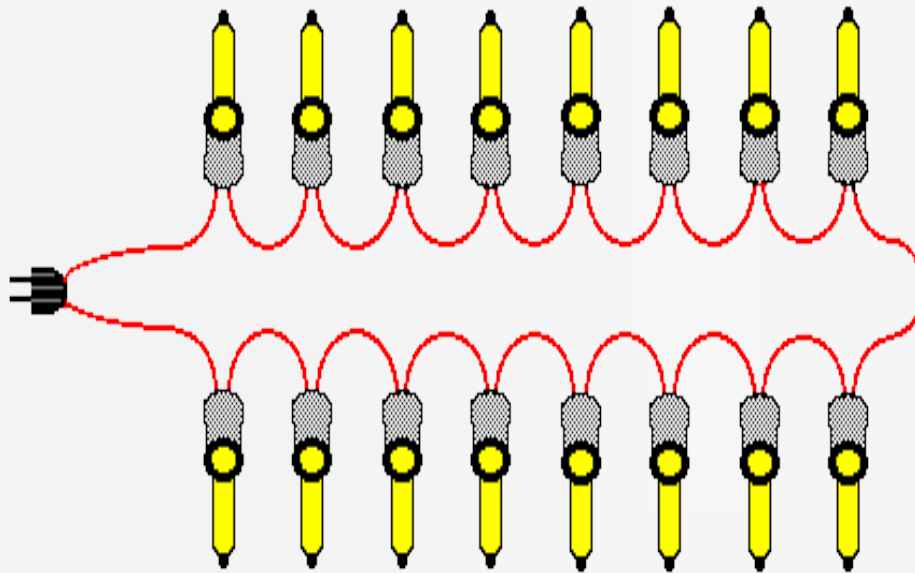

# Series Circuits

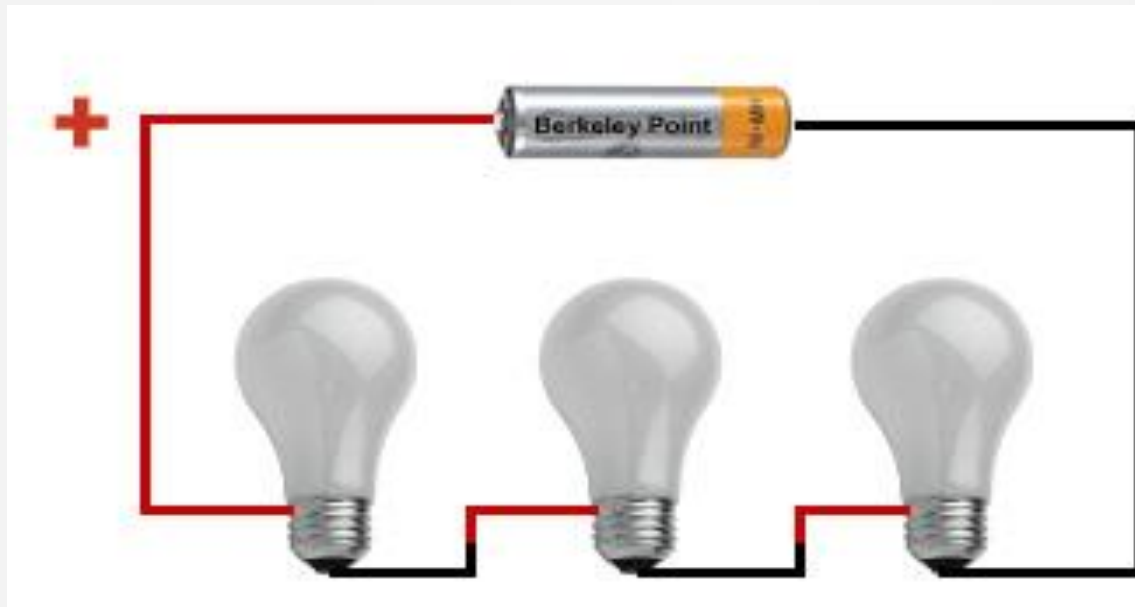





# Parallel Circuits

- In a parallel circuit, electric charge has **more than one path** that it can flow
- If **one** element stops functioning in a parallel circuit, the rest of the elements **still can operate**.


# Parallel Circuits

Example:



New Christmas Tree Lights

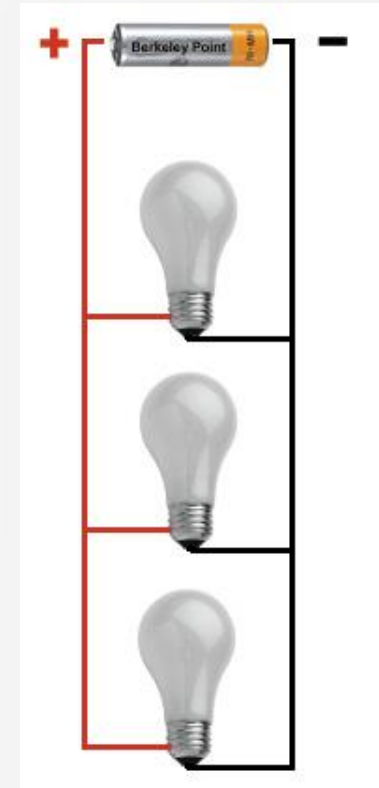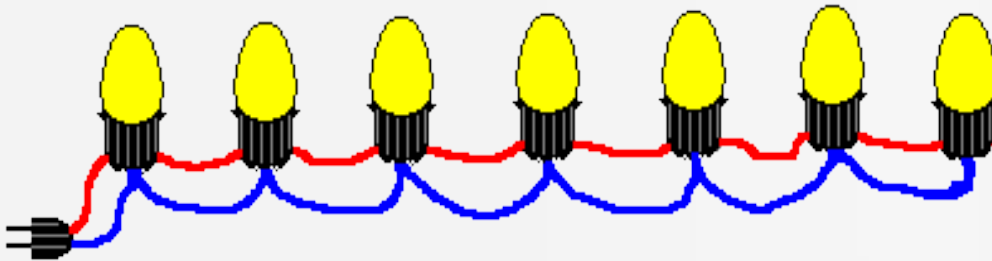

# Parallel Circuits

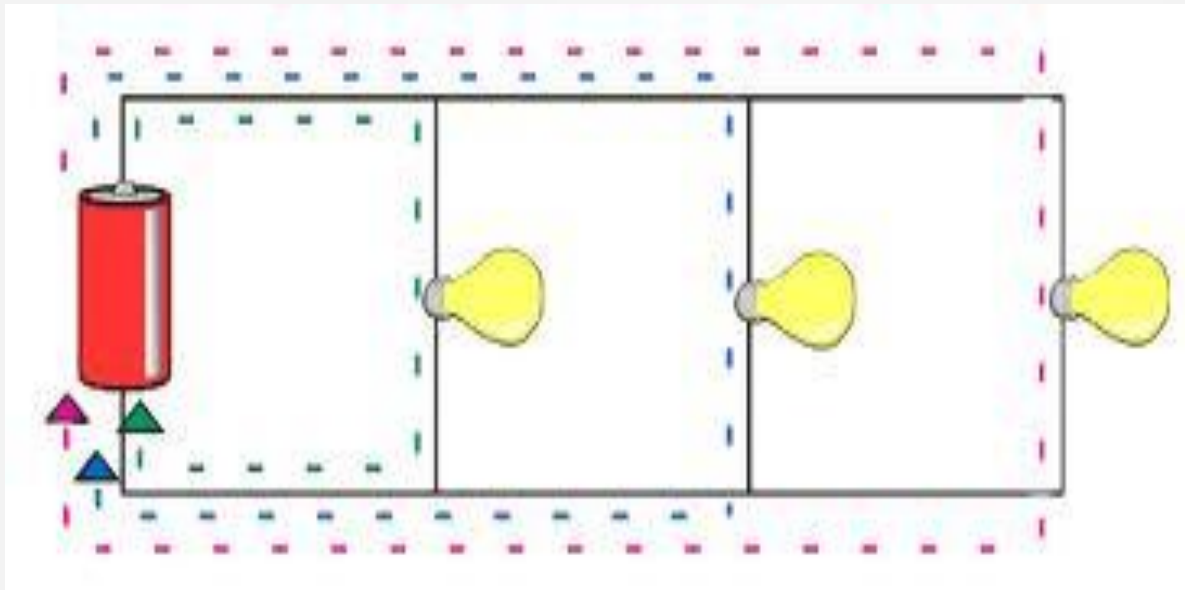

# What kind of circuit?

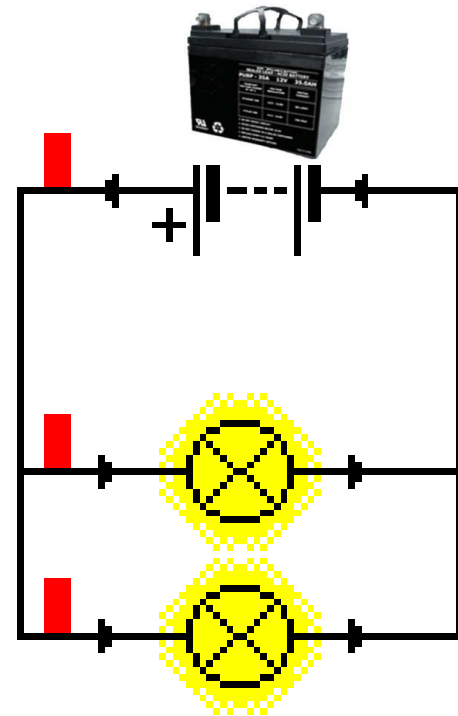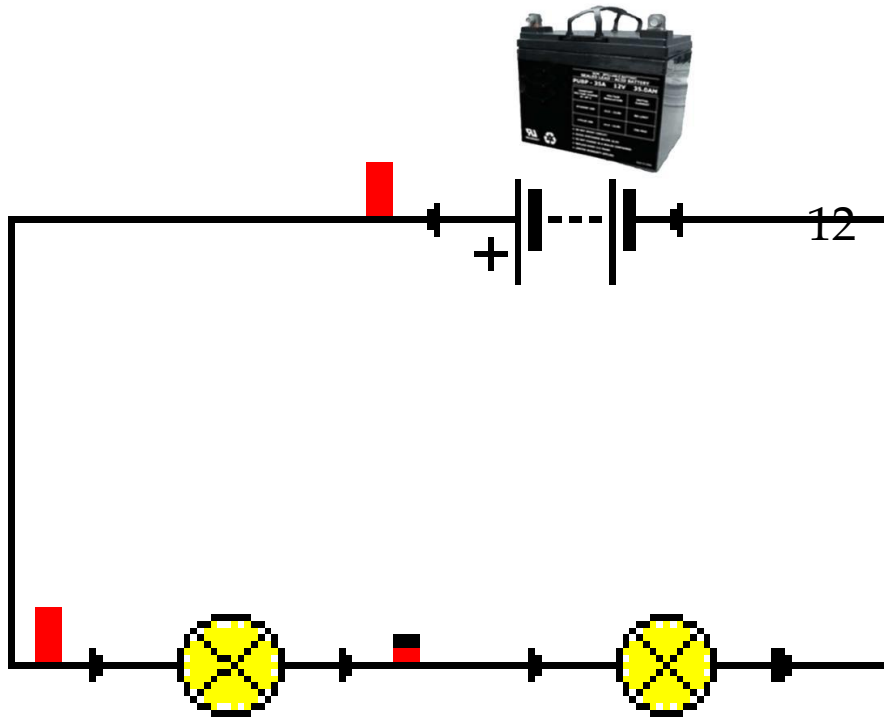

**CONCEPT  
CHECK**

What is the difference between a series and parallel circuit?


*Series:* *Only one path for the current to flow*

*Parallel:* *More than one path for the current to flow.*

# 18.4 Assessment
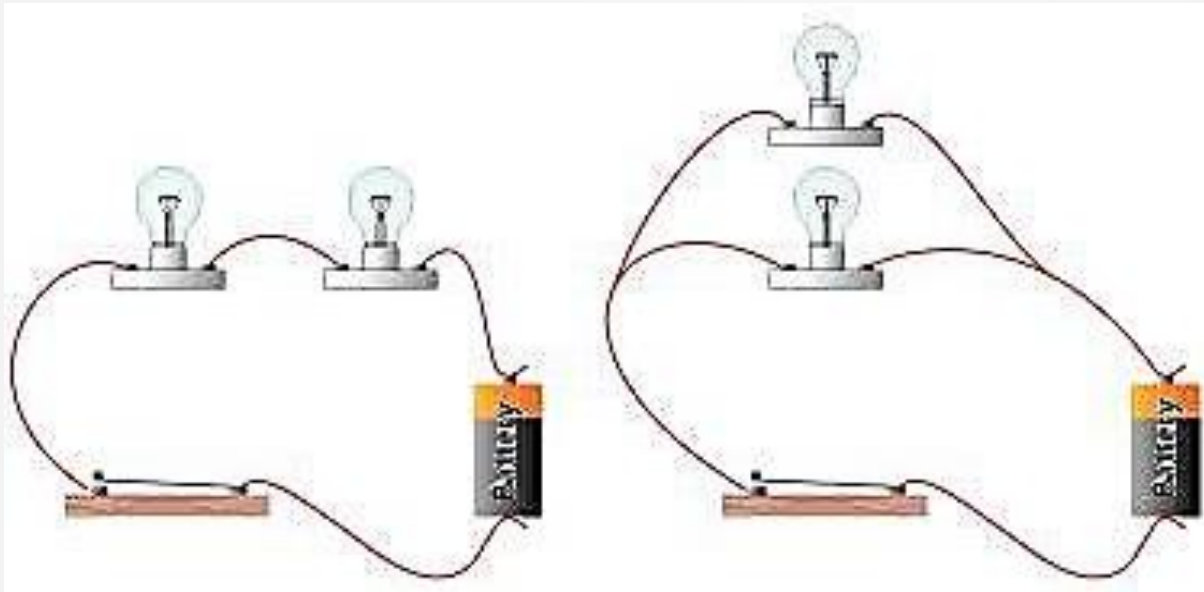
## Question #1







Identify each circuit as either a series circuit or a parallel circuit.



# 18.4 Assessment
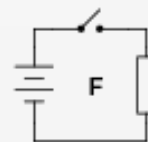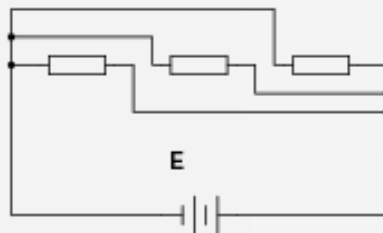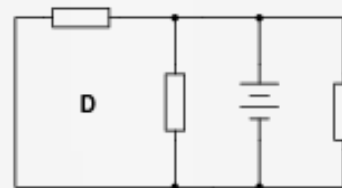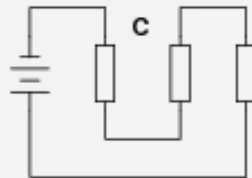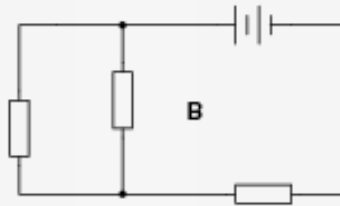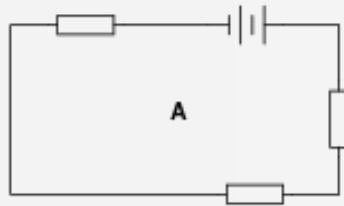
## Question #2


Identify each circuit as either a series circuit or a parallel circuit.



# 18.4 Assessment
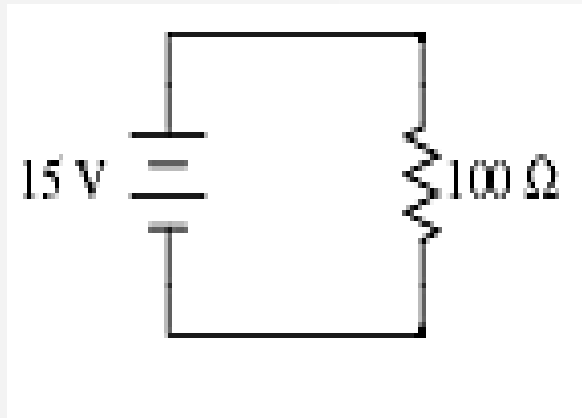
## Question #3

- Identify the type of circuit
- Using Ohm's Law, calculate the current in the circuit.





# 18.4 Assessment

## Question #4

**Name two elements that are included in a circuit diagram.**

# 18.4 Assessment

## Question #5

**What is needed to make charge flow through a circuit?**

# 18.4 Assessment

## Question #6

Identify which of these components are connected directly in series with each other, and which are connected directly in parallel with each other

Figure 1

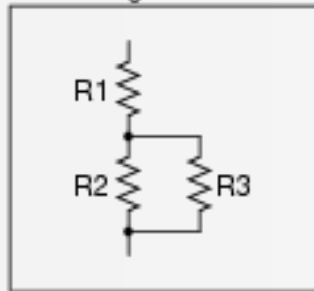


Figure 2

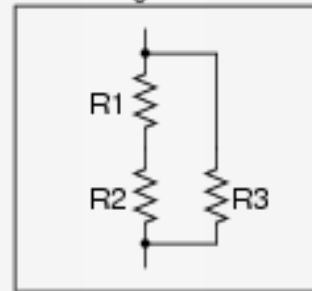


Figure 3

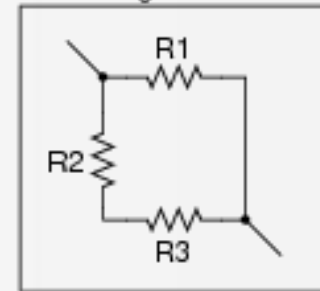


Figure 4

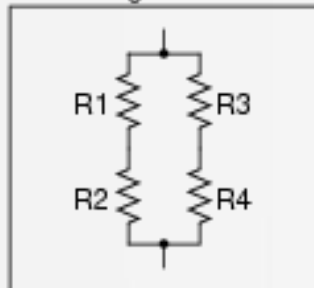


Figure 5


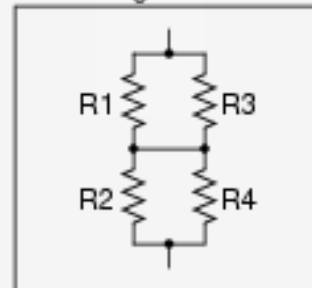


Figure 6

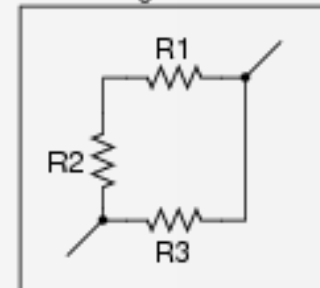

# 18.4 Assessment

## Question #7

**Draw a simple series circuit.**

# 18.4 Assessment

## Question #8

**Draw a simple parallel circuit.**