
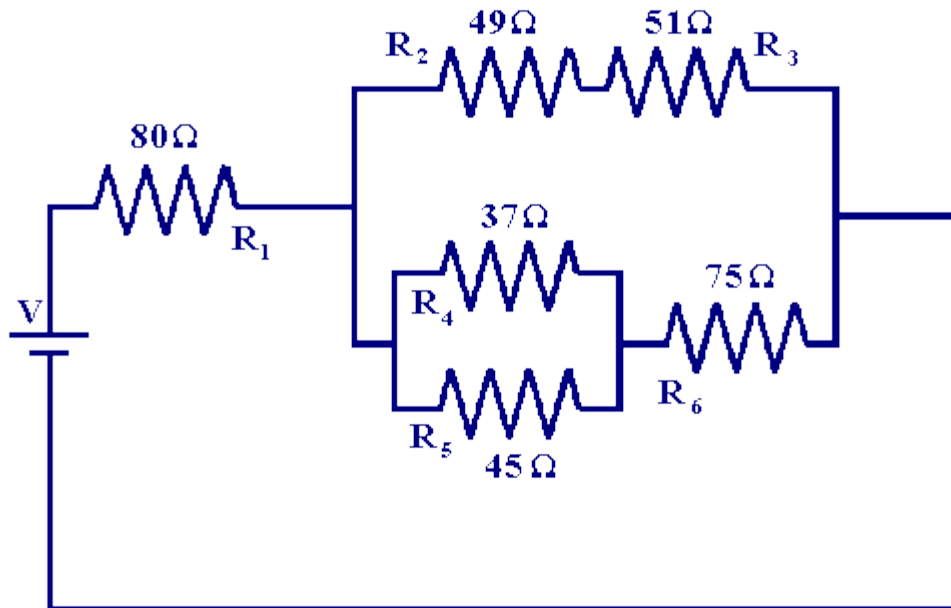


13.9

Combination Circuits Worksheet

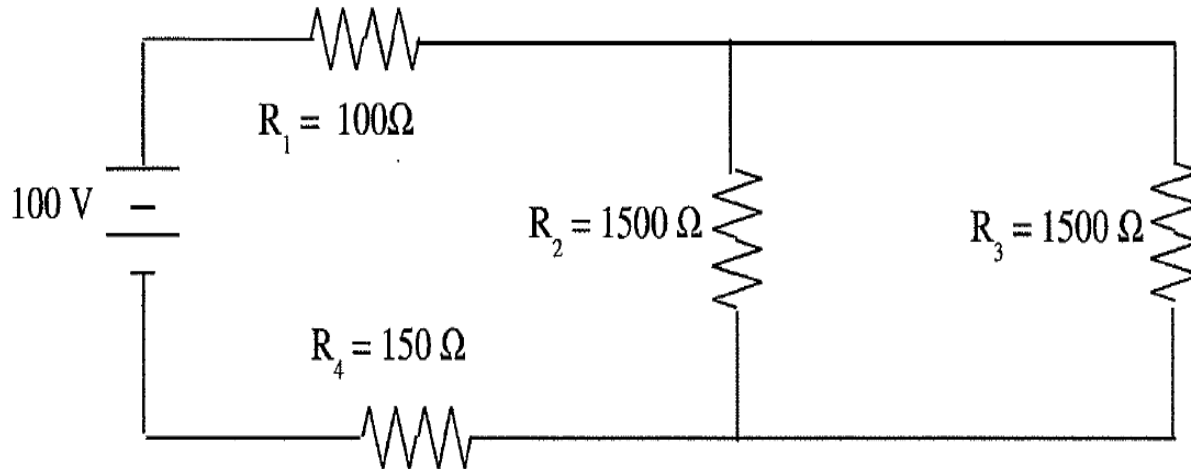

Circuit #1




Find the following:

$$R_T = \underline{1\ \text{k}\Omega}$$

$$V_T = \underline{100\ \text{V}} \quad V_1 = \underline{10\ \text{V}} \quad V_2 = \underline{75\ \text{V}} \quad V_3 = \underline{75\ \text{V}} \quad V_4 = \underline{15\ \text{V}}$$

$$I_T = \underline{100\ \text{mA}} \quad I_1 = \underline{100\ \text{mA}} \quad I_2 = \underline{50\ \text{mA}} \quad I_3 = \underline{50\ \text{mA}} \quad I_4 = \underline{100\ \text{mA}}$$

Circuit #2

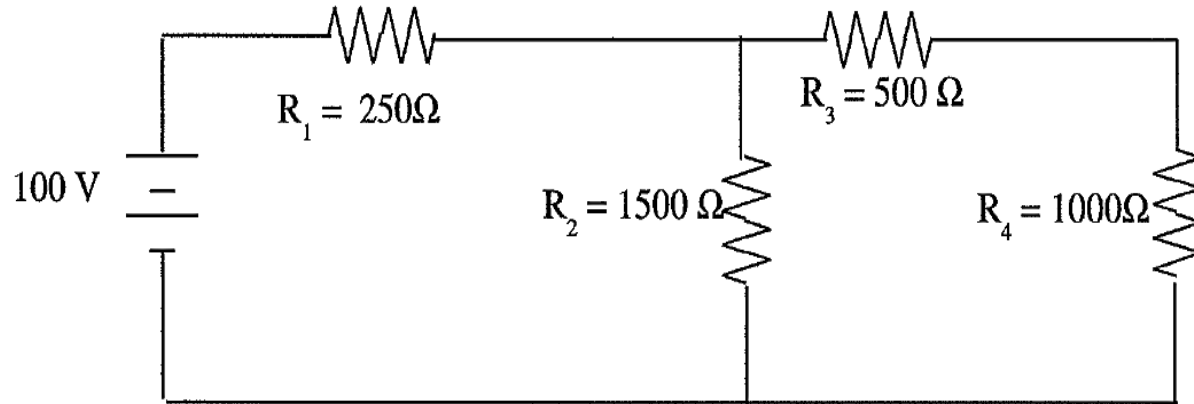

Find the following:

$$R_T = \underline{1\ \text{K}\Omega}$$

$$V_T = \underline{100\ \text{V}} \quad V_1 = \underline{25\ \text{V}} \quad V_2 = \underline{75\ \text{V}} \quad V_3 = \underline{25\ \text{V}} \quad V_4 = \underline{50\ \text{V}}$$

$$I_T = \underline{100\ \text{mA}} \quad I_1 = \underline{100\ \text{mA}} \quad I_2 = \underline{50\ \text{mA}} \quad I_3 = \underline{50\ \text{mA}} \quad I_4 = \underline{50\ \text{mA}}$$

Circuit #3

$$R_T = \underline{4 \text{ k}\Omega}$$

$$V_T = \underline{400 \text{ V}}$$

$$I_T = \underline{100 \text{ mA}}$$

$$V_1 = \underline{50 \text{ V}}$$

$$I_1 = \underline{100 \text{ mA}}$$

$$V_2 = \underline{200 \text{ V}}$$

$$I_2 = \underline{33 \text{ mA}}$$

$$V_3 = \underline{33.3 \text{ V}}$$

$$I_3 = \underline{67 \text{ mA}}$$

$$V_4 = \underline{66.7 \text{ V}}$$


$$I_4 = \underline{67 \text{ mA}}$$

$$V_5 = \underline{100 \text{ V}}$$

$$I_5 = \underline{67 \text{ mA}}$$

$$V_6 = \underline{150 \text{ V}}$$

$$I_6 = \underline{100 \text{ mA}}$$

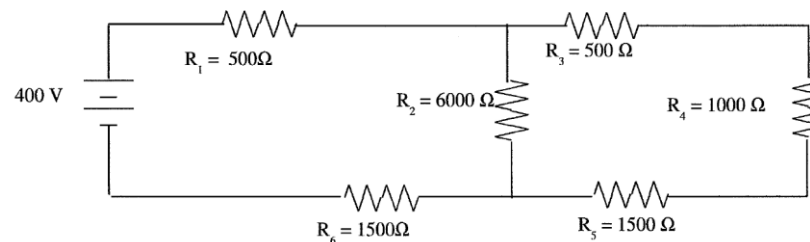

Circuit #4

$$R_T = \underline{5 \text{ k}\Omega}$$

$$V_T = \underline{100 \text{ V}}$$

$$I_T = \underline{20 \text{ mA}}$$

$$V_1 = \underline{50 \text{ V}}$$

$$I_1 = \underline{20 \text{ mA}}$$

$$V_2 = \underline{40 \text{ V}}$$

$$I_2 = \underline{4 \text{ mA}}$$

$$V_3 = \underline{16 \text{ V}}$$

$$I_3 = \underline{16 \text{ mA}}$$

$$V_4 = \underline{24 \text{ V}}$$

$$I_4 = \underline{16 \text{ mA}}$$

$$V_5 = \underline{10 \text{ V}}$$

$$I_5 = \underline{20 \text{ mA}}$$

